

# Homework No. 05 (Spring 2022)

## PHYS 203B-001: COLLEGE PHYSICS

*Department of Physics, Southern Illinois University–Carbondale*

Due date: Wednesday, 2022 Feb 23, 10:00am, on D2L

### Instructions

- To the extent to which you depend on resources to complete this homework is a measure of how much extra work you need to put in to master the related concepts.
- Describe your thought process in detail and organize it clearly. Make sure your answer has the correct units and the right number of significant digits.
- After completion, scan the pages as a single PDF file, and submit the file on D2L (Assessments → Assignments).

### Problems

1. (**10 points.**) A capacitor of capacitance  $10.0\text{ nF}$  is connected to a  $10.0\text{ V}$  battery. Let us assume that the capacitor consists of two parallel plates of area  $A$  separated by distance  $d$ .
  - (a) Determine the charge accumulated on each plate of the capacitor.
  - (b) Determine the energy stored in the capacitor.

#### Solution

2. (**10 points.**) Determine the equivalent capacitance between points  $A$  and  $B$  in the circuit in Figure 1. Given  $C_1 = 1.0\ \mu\text{F}$ ,  $C_2 = 2.0\ \mu\text{F}$ ,  $C_3 = 3.0\ \mu\text{F}$ , and  $C_4 = 4.0\ \mu\text{F}$ .

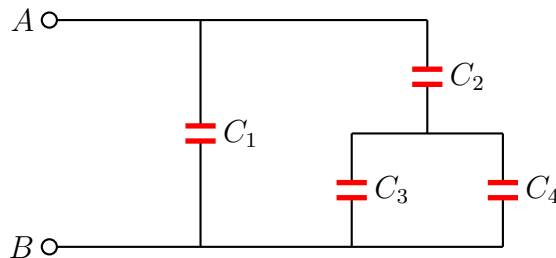


Figure 1: Problem 2

#### Solution

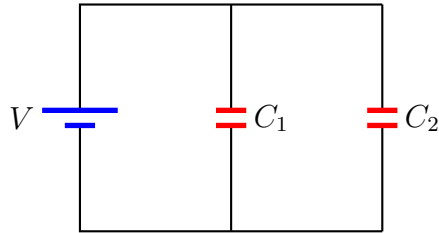


Figure 2: Problem 3

3. (10 points.) A potential difference  $V = 10.0 \text{ V}$  is applied across a capacitor arrangement with two capacitances connected in parallel,  $C_1 = 10.0 \mu\text{F}$  and  $C_2 = 20.0 \mu\text{F}$ .
- Find the equivalent capacitance.
  - Find the charges  $Q_1$  and  $Q_2$  on each of the capacitors.
  - Find the voltages  $V_1$  and  $V_2$  across each of the capacitors.
  - Find the potential energies  $U_1$  and  $U_2$  stored inside each of the capacitors.
  - Find the ratio  $V_1/V_2$  of the voltages across the capacitors.
  - Find the ratio  $Q_1/Q_2$  of the charges on the capacitors.
  - Find the ratio  $U_1/U_2$  of the potential energies stored inside the capacitors.

### Solution

4. (10 points.) A potential difference  $V = 10.0 \text{ V}$  is applied across a capacitor arrangement with two capacitances connected in series,  $C_1 = 10.0 \mu\text{F}$  and  $C_2 = 20.0 \mu\text{F}$ .

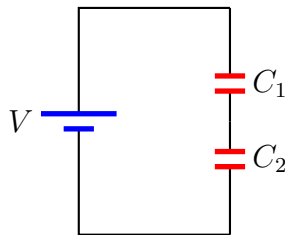


Figure 3: Problem 4

- Find the equivalent capacitance.
- Find the charges  $Q_1$  and  $Q_2$  on each of the capacitors.
- Find the voltages  $V_1$  and  $V_2$  across each of the capacitors.
- Find the potential energies  $U_1$  and  $U_2$  stored inside each of the capacitors.
- Find the ratio  $V_1/V_2$  of the voltages across the capacitors.

- (f) Find the ratio  $Q_1/Q_2$  of the charges on the capacitors.  
(g) Find the ratio  $U_1/U_2$  of the potential energies stored inside the capacitors.

**Solution**

5. (10 points.) Estimate the drift velocity of conduction electrons in a copper wire of radius 1.0 mm using

$$I = neAv_d. \quad (1)$$

Copper has one free electron per atom available for conduction. For reference copper wire has  $9 \times 10^{28}$  atoms/m<sup>3</sup>. Use  $I = 1.0$  A. How much time (in hours) does it take for an individual electron to begin from the light switch and reach the bulb that is connected by a 2.0 m long copper wire?

**Solution**

6. (10 points.) Watt is the unit of power. Watt-hour is a unit of energy. How much is kWh (kilo Watt-hour) in Joules? The average cost of electricity in the United States, for residential users, is about 0.15 USD/kWh (15 cents per kiloWatt-hour). At this rate your electricity bill for a month came out to be 50.00 USD. How much electric energy (in Joules) did you use in the month?

**Solution**

7. (10 points.) Resistance is inversely proportional to the area of crosssection  $A$  and proportional to the length  $l$ , such that

$$R = \frac{\rho l}{A}, \quad (2)$$

where  $\rho$  is the resistivity of the material. A cylindrical copper rod has resistance  $R$ . It is reformed to thrice its original length with no change of volume. What is its new resistance in terms of the original resistance  $R$ ?

**Solution**

8. (10 points.) Figure 4 shows three resistors connected in parallel to a battery. The battery has a voltage of  $V = 10.0$  V, and the resistors have equal resistances of  $R = 300.0 \Omega$ .
- (a) Determine the equivalent resistance across the battery.
  - (b) Determine the voltage across each of the resistor.
  - (c) Determine the current passing through each resistor.
  - (d) Determine the power consumed by each resistor.

**Solution**

9. (10 points.) Figure 5 shows two resistors connected in series to a battery. The battery has a voltage of  $V = 10.0$  V, and the resistors have resistances  $R_1 = 100.0 \Omega$  and  $R_2 = 200.0 \Omega$ .

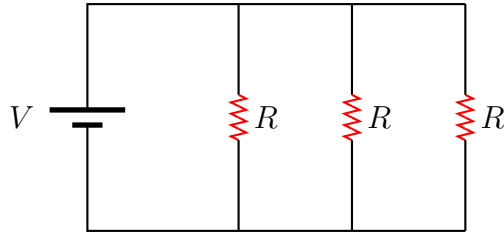


Figure 4: Problem 8

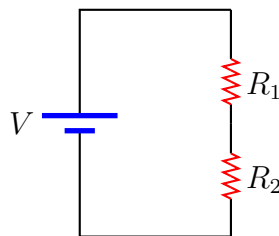


Figure 5: Problem 9

- (a) Determine the equivalent resistance across the battery.
- (b) Determine the voltage across each of the resistor.
- (c) Determine the current passing through each resistor.
- (d) Determine the power consumed by each resistor.
- (e) Find the ratio  $P_1/P_2$  of the powers of the resistors.
- (f) If the resistors represented electric bulbs, which bulb would glow brighter?

**Solution**

10. (**10 points.**) Figure 6 shows two resistors connected in parallel to a battery. The battery has a voltage of  $V = 10.0 \text{ V}$ , and the resistors have resistances  $R_1 = 100.0 \Omega$  and  $R_2 = 200.0 \Omega$ .

- (a) Determine the equivalent resistance across the battery.
- (b) Determine the voltage across each of the resistor.
- (c) Determine the current passing through each resistor.
- (d) Determine the power consumed by each resistor.
- (e) Find the ratio  $P_1/P_2$  of the powers of the resistors.
- (f) If the resistors represented electric bulbs, which bulb would glow brighter?

**Solution**

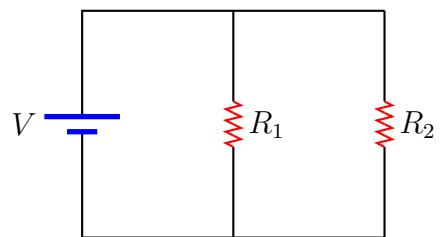


Figure 6: Problem 10